
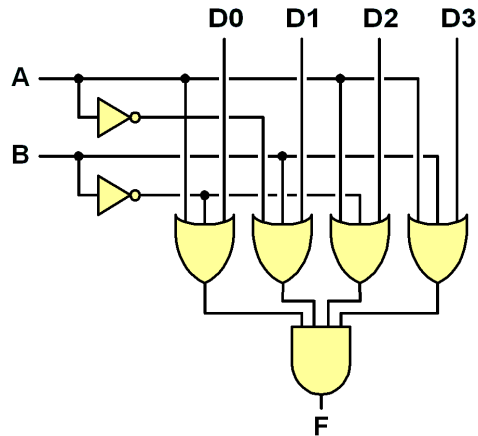


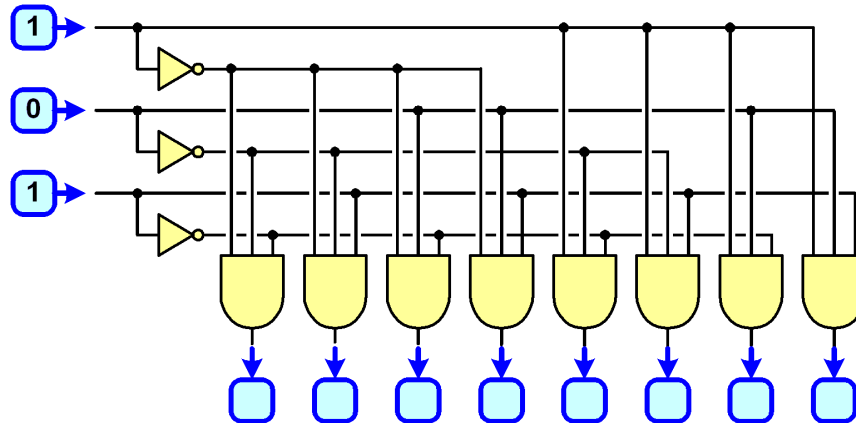
1. **Identify the errors** in the following multiplexer circuit:



2. **Show the outputs** of the following decoder circuit based on the given inputs:



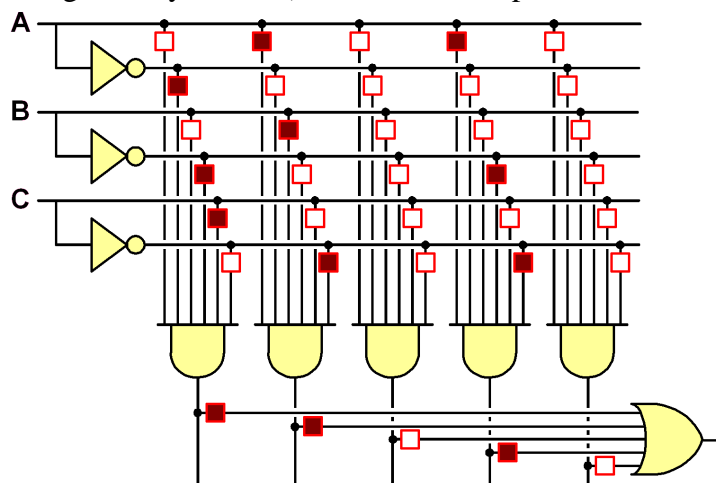3. **Write a Boolean expression** that shows what is being done by the following Programmable Logic Array circuit (filled-in boxes represent connected fuses).



4. **What happens** to the value of a binary number when it's put through a shifter circuit that moves all the bits one position to the **right**?
5. Use a **multiplexer** to create a circuit that produces an **even parity output** for **three input bits**. In other words, the output should be **TRUE** if the number of **TRUE** inputs is **odd**.
6. **Fill in** the following truth table for a **full adder**:

A	B	Carry In	Sum	Carry Out
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

7. An 8-bit ALU has the following numbers present on it's A and B inputs:

0	1	0	0	1	0	1	1
A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀

0	0	1	1	0	1	0	1
B ₇	B ₆	B ₅	B ₄	B ₃	B ₂	B ₁	B ₀

Show what the ALU outputs will be given the following control inputs:

F0	F1	ENA	ENB	INVA	INC
0	0	1	1	0	0

O ₇	O ₆	O ₅	O ₄	O ₃	O ₂	O ₁	O ₀

1	1	1	1	0	0
---	---	---	---	---	---

--	--	--	--	--	--	--	--

1	0	1	0	1	1
---	---	---	---	---	---

--	--	--	--	--	--	--	--

8. Convert the following decimal numbers to **8-bit signed binary numbers** :

87

-92

9. Convert the following **8-bit signed binary numbers** to decimal:

1 0 1 1 0 1 0 1

0 1 0 1 1 0 1 1