
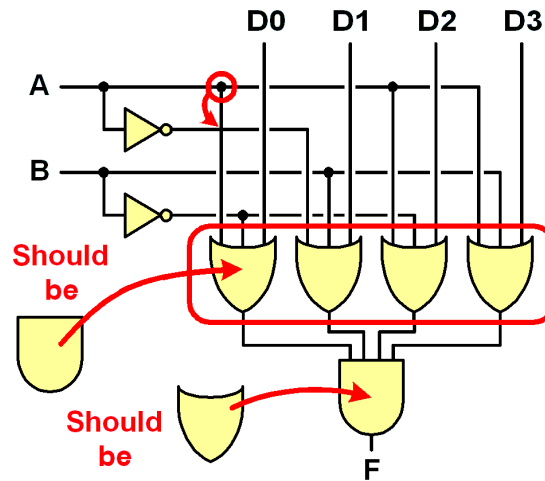


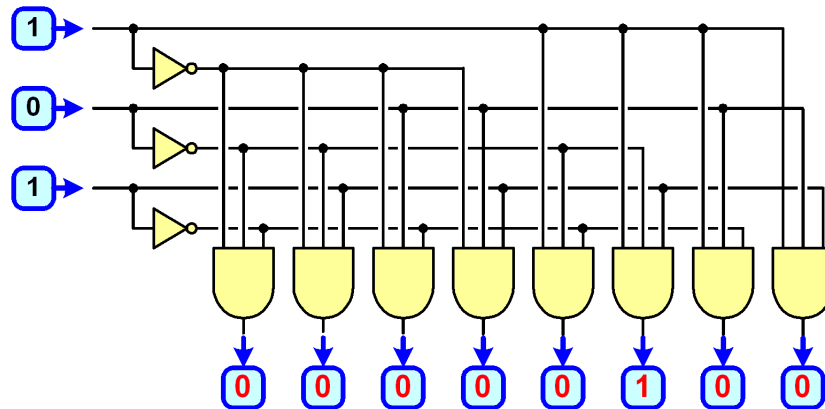
1. **Identify the errors** in the following multiplexer circuit:



2. **Show the outputs** of the following decoder circuit based on the given inputs:



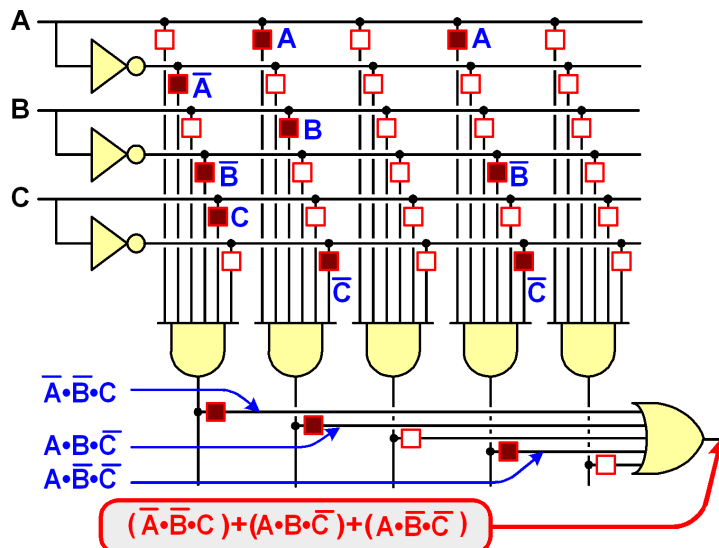
3. **Write a Boolean expression** that shows what is being done by the following Programmable Logic Array circuit (filled-in boxes represent connected fuses).



4. **What happens** to the value of a binary number when it's put through a shifter circuit that moves all the bits one position to the **right**?

**The value is divided by 2**

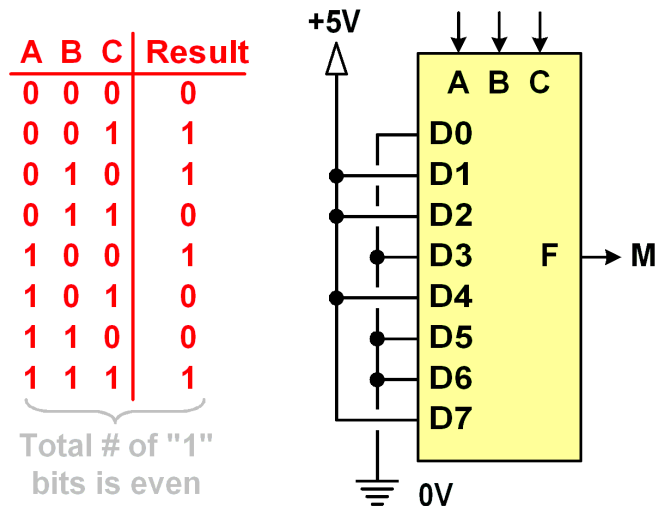5. Use a **multiplexer** to create a circuit that produces an **even parity output** for **three input bits**. In other words, the output should be **TRUE** if the number of **TRUE** inputs is **odd**.



6. **Fill in** the following truth table for a **full adder**:

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

7. An 8-bit ALU has the following numbers present on it's A and B inputs:

0	1	0	0	1	0	1	1	0	0	1	1	0	1	0	1
A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	B <sub>7</sub>	B <sub>6</sub>	B <sub>5</sub>	B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>

Show what the ALU outputs will be given the following control inputs:

F0	F1	ENA	ENB	INVA	INC	O <sub>7</sub>	O <sub>6</sub>	O <sub>5</sub>	O <sub>4</sub>	O <sub>3</sub>	O <sub>2</sub>	O <sub>1</sub>	O <sub>0</sub>
0	0	1	1	0	0	0	0	0	0	0	0	0	1
1	1	1	1	0	0	1	0	0	0	0	0	0	0
1	0	1	0	1	1	1	1	1	1	1	1	1	1

8. Convert the following decimal numbers to **8-bit signed binary numbers** :

128	64	32	16	8	4	2	1
0	1	0	1	0	1	1	1

87 = 64 + 16 + 4 + 2 + 1

128	64	32	16	8	4	2	1
0	1	0	1	1	1	0	0
↓	↓	↓	↓	↓	↓	↓	↓
1	0	1	0	0	0	1	1
↓	↓	↓	↓	↓	↓	↓	↓
1	0	1	0	0	1	0	0

-92 =

9. Convert the following **8-bit signed binary numbers** to decimal:

1	0	1	1	0	1	0	1
↓	↓	↓	↓	↓	↓	↓	↓
0	1	0	0	1	0	1	0
↓	↓	↓	↓	↓	↓	↓	↓
0	1	0	0	1	0	1	1

64 + 8 + 2 + 1 = 75  
so original number is -75

0	1	0	1	1	0	1	1
↓	↓	↓	↓	↓	↓	↓	↓
0	1	0	1	1	0	1	1

64 + 16 + 8 + 2 + 1 = 91